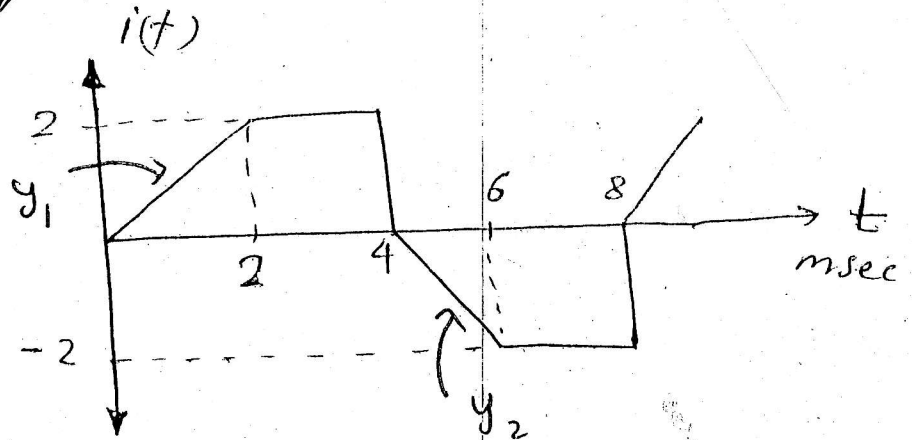
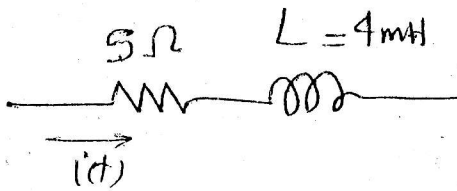


750

Find $V_R(t)$, $V_L(t)$, V_{total} 

سنترفكره

وزارة التعليم - المملكة العربية السعودية
1122-7777-1007778808

$$i(t) = \begin{cases} t & 0 \leq t \leq 2 \\ 2 & 2 \leq t \leq 4 \\ -t + 4 & 4 \leq t \leq 6 \\ -2 & 6 \leq t \leq 8 \end{cases}$$

$$y_1 = t + C_1$$

$$y_1(0) = 0 \rightarrow C_1 = 0$$

$$y_2' = -t + C_2$$

$$y_2(4) = 0 = -4 + C_2$$

$$\therefore C_2 = 4$$

$$V_R(t) = I(t) * R$$

$$V_R(t) = \begin{cases} 5t & 0 \leq t \leq 2 \\ 10 & 2 \leq t \leq 4 \\ -5t + 20 & 4 \leq t \leq 6 \\ -10 & 6 \leq t \leq 8 \end{cases}$$

$$V_L(t) = L \frac{di}{dt}$$

$$i_L(t) = 4 \text{ mA} *$$




$$\begin{cases} 1 & 0 \leq t \leq 2 \\ 0 & 2 \leq t \leq 4 \\ -1 & 4 \leq t \leq 6 \\ 0 & 6 \leq t \leq 8 \end{cases}$$

$$v_L(t) = \begin{cases} 4 \text{ m} & 0 \leq t \leq 2 \\ 0 & 2 \leq t \leq 4 \\ -4 \text{ m} & 4 \leq t \leq 6 \\ 0 & 6 \leq t \leq 8 \end{cases}$$




$$v(t) = v_R + v_L \approx v_R$$

$$v_t =$$
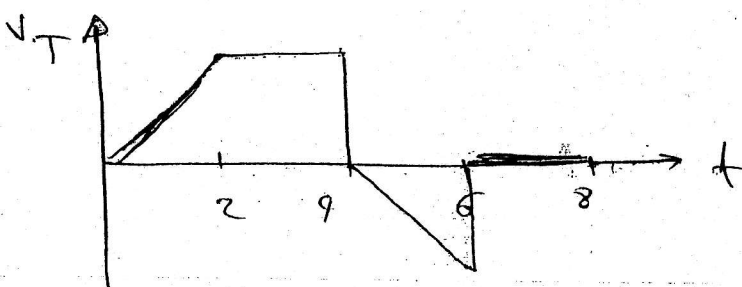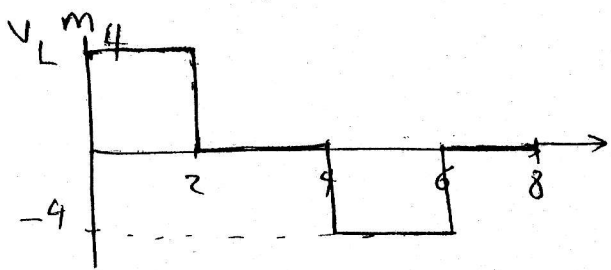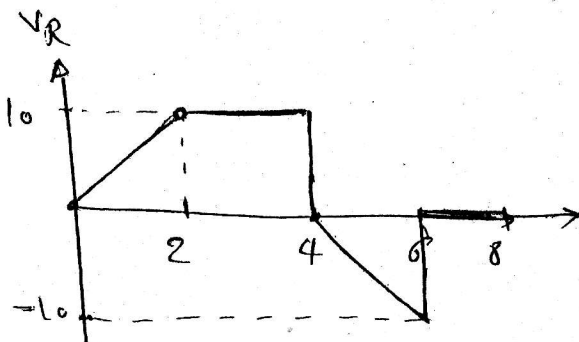
$$\begin{cases} 5t + 4 \text{ m} & 0 \leq t \leq 2 \\ 10 & 2 \leq t \leq 4 \\ -5t + 20 - 4 \text{ m} & 4 \leq t \leq 6 \\ -10 & 6 \leq t \leq 8 \end{cases}$$




②

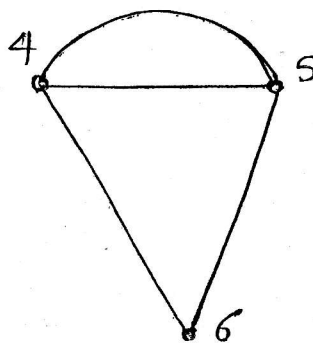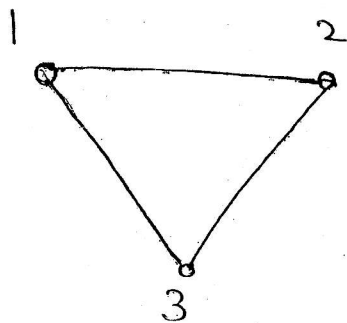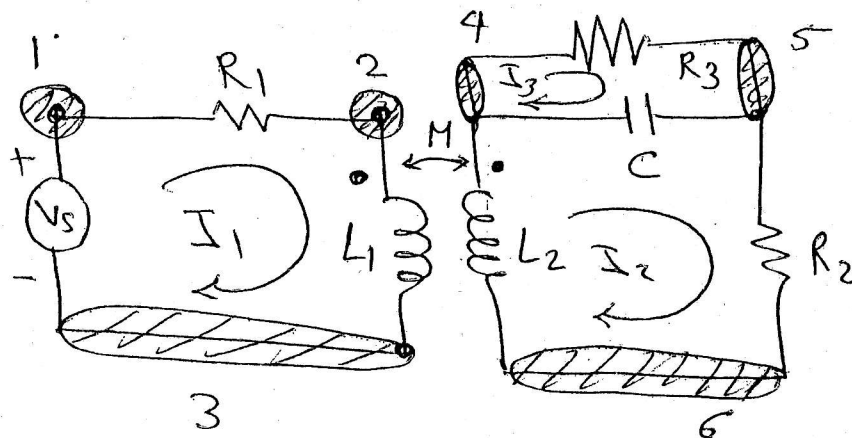

Loop 1 :-

$$V_S = I_1 R_1 + V_{L1}$$
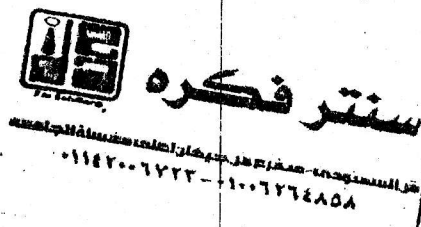
$$V_{L1} = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$



* K.V.L for Loop 2 :-


$$0 = V_{L2} + R_2 I_2 + \frac{1}{C} \int (I_2 - I_3) dt$$

$$V_{L2} = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

K.V.L for Loop 3:

$$0 = I_3 R_3 + \frac{1}{C} \int (I_3 - I_2) dt$$

③

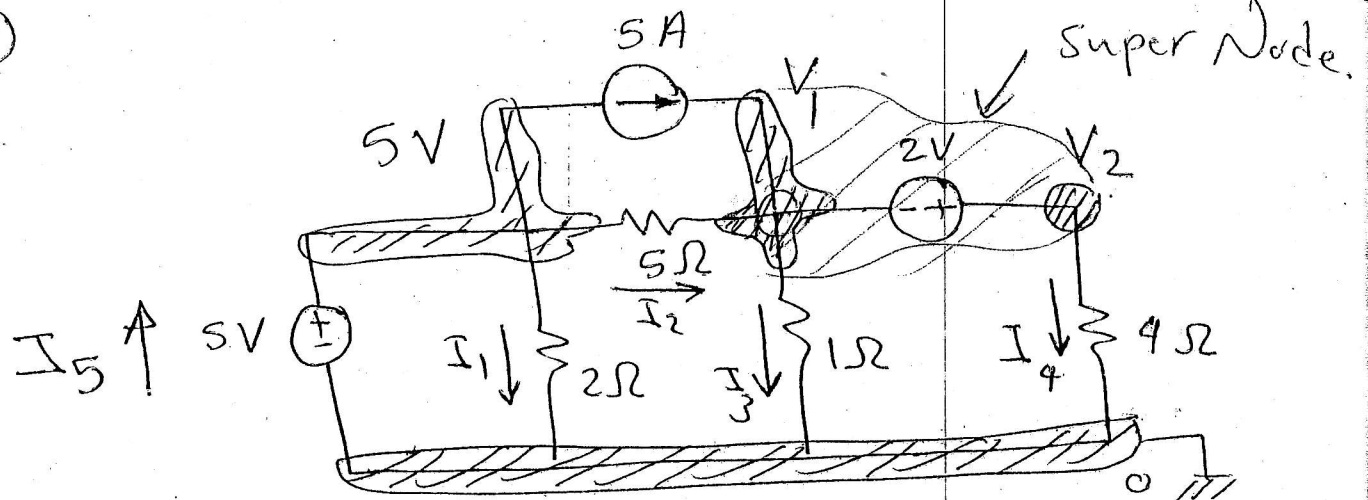

$$2 = V_2 - V_1 \longrightarrow \textcircled{1}$$

* K.C.L at Super Node:-

$$5 = \frac{V_1 - 5}{5} + \frac{V_1 - 0}{1} + \frac{V_2 - 0}{4}$$

$$6 = V_1 \left(\frac{1}{5} + 1 \right) + \frac{V_2}{4} \longrightarrow \textcircled{2}$$

$$V_1 = 3.79 \text{ V}$$

$$V_2 = 5.79 \text{ V}$$

$$I_1 = \frac{5}{2} = 2.5 \text{ A}, \quad I_2 = \frac{5 - 3.79}{5\Omega} = \frac{1.21}{5} \text{ A} = 0.24 \text{ A}$$

$$I_3 = \frac{3.79}{1} = 3.79 \text{ A}, \quad I_4 = \frac{5.79}{4} = 1.44$$


$$P_{5\Omega} = I_2^2 \times 5$$

$$P_{1\Omega} = I_3^2 \times 1$$

$$P_{4\Omega} = I_4^2 \times 4$$

$$P_{5A} = 5 \times (5 - 3.79)$$

$$P_{2V} = -2 \times I_4$$

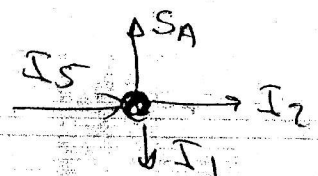

$$I_5 = I_1 + I_2 + I_3$$


$$P_{SV} = -S \times I_5$$



سنترفكره

مركز البحوث والدراسات
٠١٤٢٠٦٧٢٢ - ٠١٠٠٦٢٦٤٨٥٨


(4)

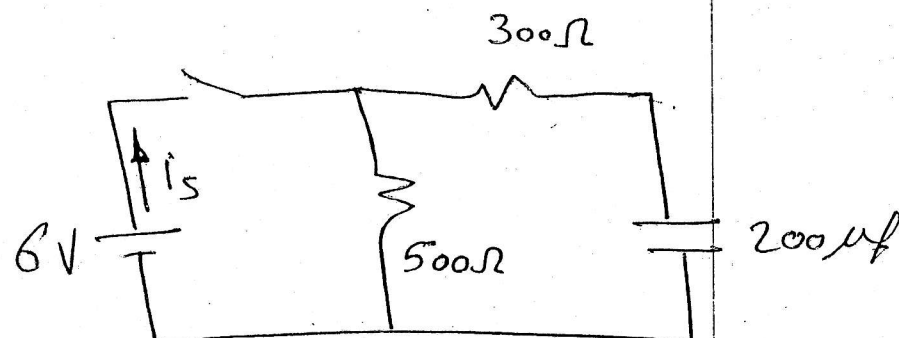

$t < 0 \rightarrow$ initial value

$$i(0) = \frac{6}{300 // 500}$$

$$= \frac{6}{187.5} = 32 \text{ mA}$$

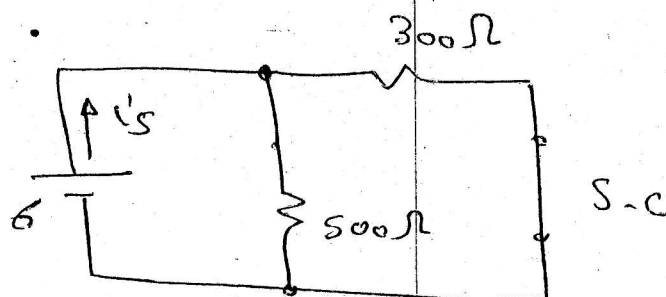

$$i(t) = i_c(t) + i_p(t)$$

$$i_c(t) = K e^{-\frac{t}{\tau}}$$

$$i_c(t) = K e^{-\frac{t}{60 \text{ ms}}}$$

$$\underline{i_p(t)}$$

$$i_p(t) = \frac{6}{500} = 12 \text{ mA}$$

$$\tau = RC$$

$$= 300 \times 200 \mu\text{F}$$

$$= 60 \text{ ms}$$

$$i(t) = i_c(t) + i_p(t)$$

$$i(t) = K e^{\frac{-t}{60ms}} + 12mA$$


$$i(0) = 32mA = K e^0 + 12mA \rightarrow K = 20mA$$

$$\therefore i(t) = 20mA e^{\frac{-t}{60ms}} + 12mA$$

$$i(60ms) = 20mA e^{\frac{-60ms}{60ms}} + 12mA$$

$$= 19.35 mA$$

5

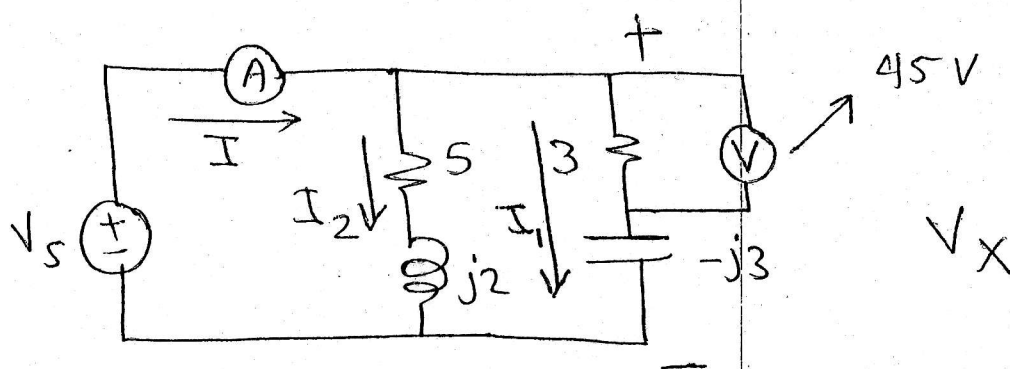

$$I_1 = \frac{V}{3} = \frac{45}{3} = 15$$

$$V_X = I_1 \times (3 - j3) = 15 (3 - j3)$$

$$= 45 - j45$$

$$I_2 = \frac{V_X}{5 - j2} = \frac{45 - j45}{5 - j2}$$

$$I = I_1 + I_2$$

$$V_S = V_X$$


$$\therefore P_S = -V_S \cdot I$$



سنتر فکرة

شماره تماس: ۰۱۱۴۲۰۰۶۷۲۲ - ۰۱۰۰۶۷۶۴۸۵۸
شماره فکس: ۰۱۱۴۲۰۰۶۷۲۲ - ۰۱۰۰۶۷۶۴۸۵۸

7

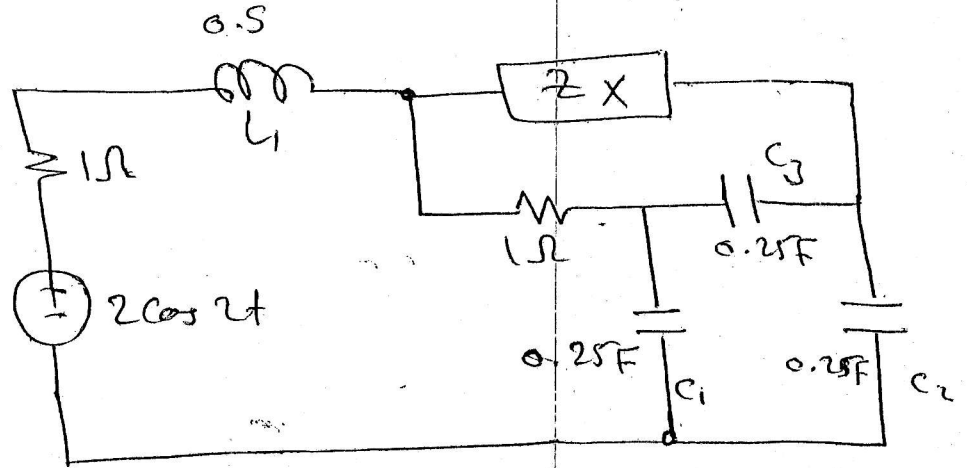


$$2 \cos 2t = 2 \sin 2t + 90$$

$$X_{L1} = j\omega L_1 = j$$

$$X_{C1} = \frac{1}{j\omega C_1} = -j2$$


$$X_{C2} = -j2$$



$$X_{C3} = -j2$$

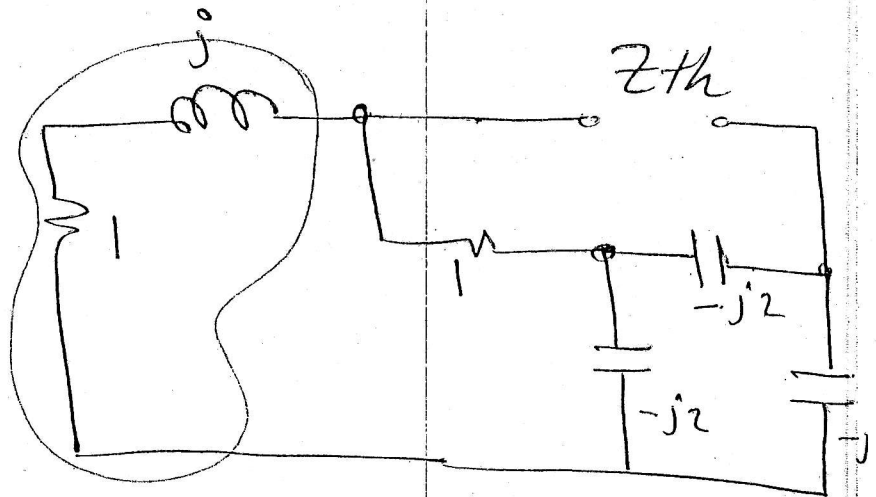

سنتر فکرة

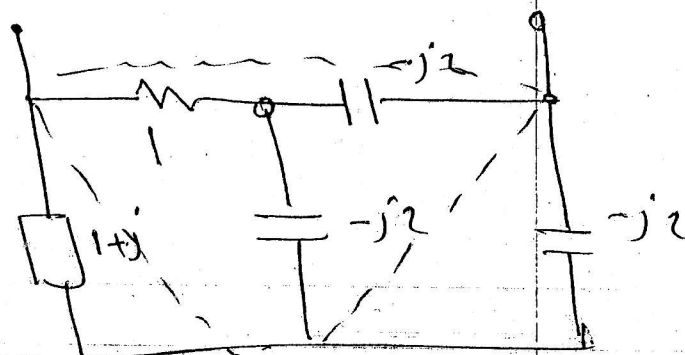شماره تماس: ۰۱۱۴۲۰۰۶۷۲۲ - ۰۱۰۰۶۷۶۴۸۵۸
شماره فکس: ۰۱۱۴۲۰۰۶۷۲۲ - ۰۱۰۰۶۷۶۴۸۵۸



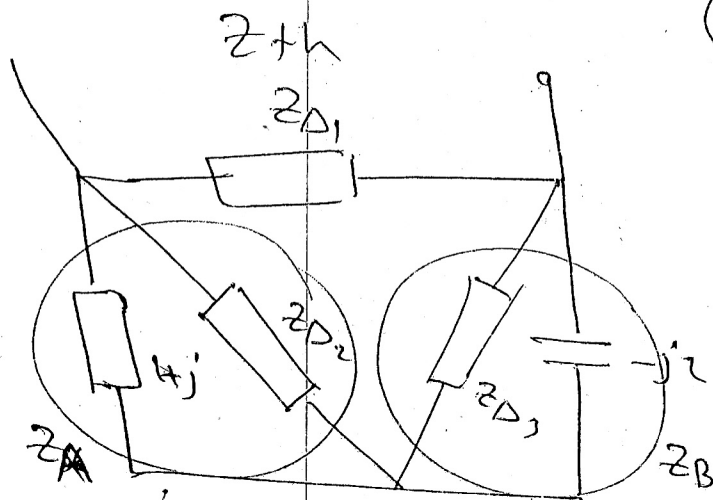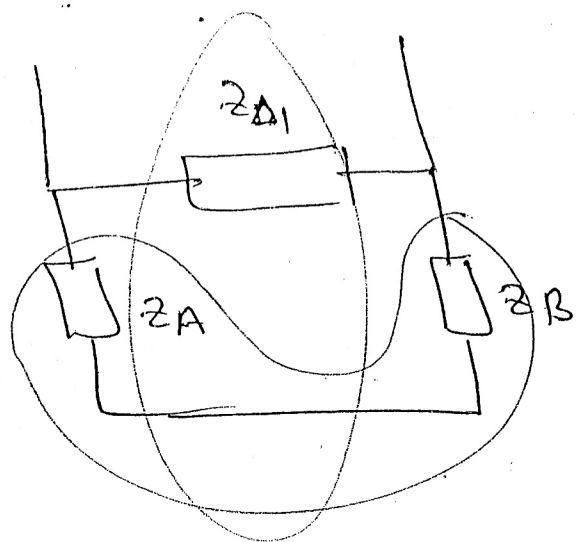


$$Z_{th} = (Z_A + Z_B) \parallel Z_{\Delta 1}$$

$$P_{max} = \frac{|V_{th}|^2}{4 \operatorname{Re}\{Z_x\}}$$



سترفكره

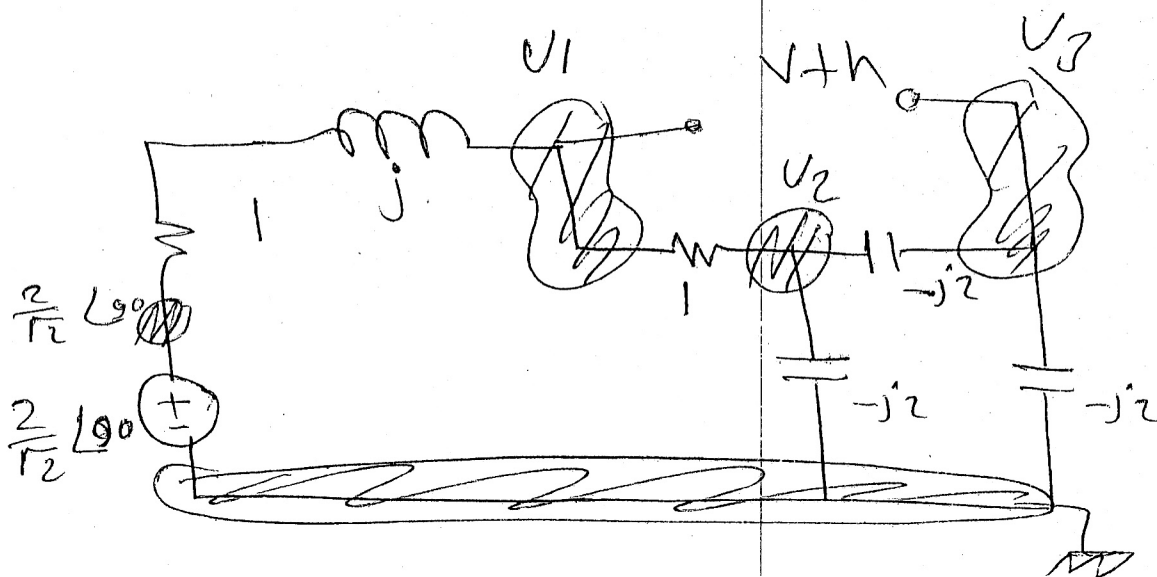شركة التصميم والهندسة الكهربائية
٠١٤٢٠٠٦٧٢٢ - ٠١٠٠٦٢٦٤٨٥٨



KCL at V_1

$$0 = \frac{V_1 - \frac{2}{12} \angle 90^\circ}{1 + j} + \frac{V_1 - V_2}{1}$$

KCL for Node V_2

$$0 = \frac{V_2 - 0}{-j2} + \frac{V_2 - V_3}{-j2} + \frac{V_2 - V_1}{1}$$

K.cl at V_3

$$0 = \frac{V_3 - 0}{-j2} + \frac{V_3 - V_2}{-j2}$$

بدل لے کر، V_1, V_2, V_3 نو صاف

$$\therefore V_{th} = V_1 - V_3$$



سینٹر فیکرہ

قرآن مجید کی تفسیر اور تعلیمی اداروں کے لیے
۰۱۱۴۲۰۰۶۷۲۲ - ۰۱۰۰۶۷۶۸۵۸

6


Find V_x

$$10 \cos 2t$$


$$10 \angle 0^\circ (2 + j90)$$

Using Superpos

$$V_x = V_{x1} + V_{x2} + V_{x3}$$

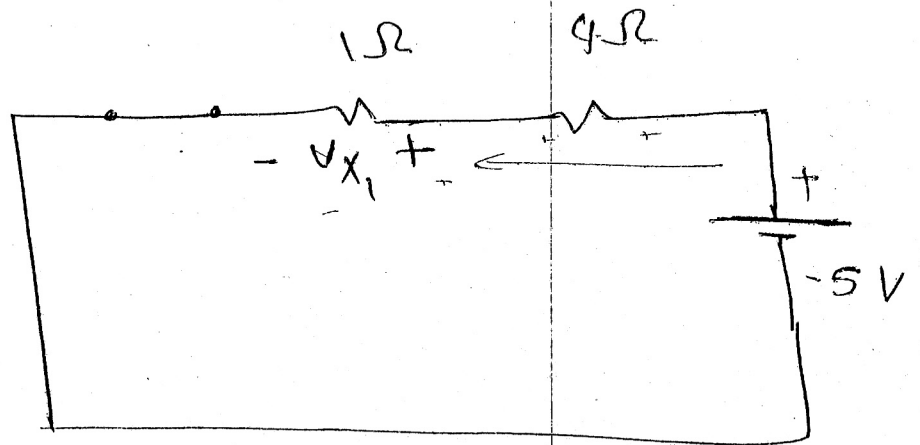


$$V_{x1} = 5 \times \frac{1}{5} = 1V$$


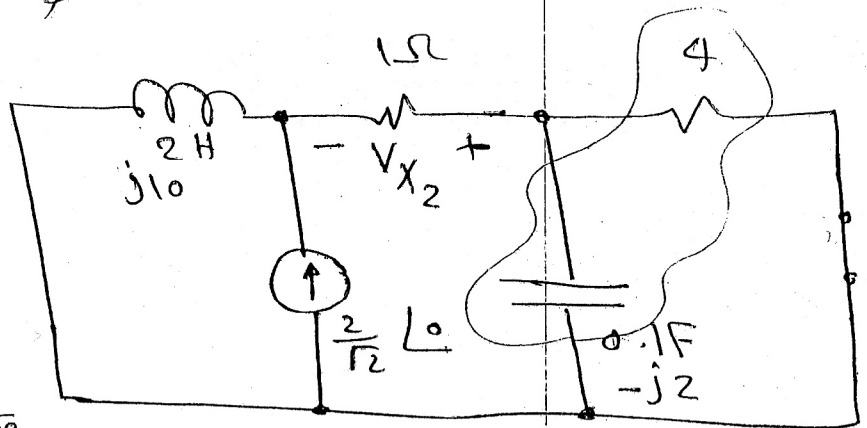


$$I_x = \frac{2}{12} \angle 0^\circ \times \frac{j10}{j10 + 1 \frac{-j8}{4-j2}}$$

$$V_{x2} = -I_x \times 1\Omega$$

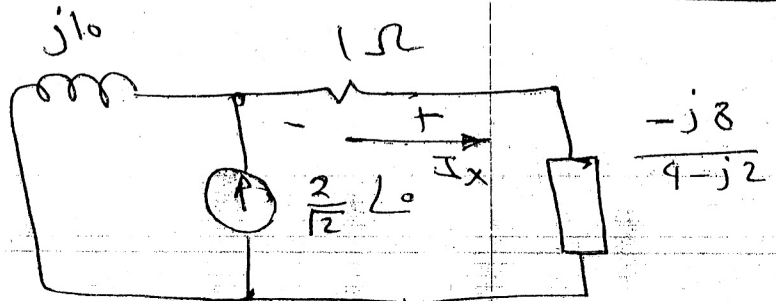


$$\frac{10}{\sqrt{2}} \angle 0^\circ$$

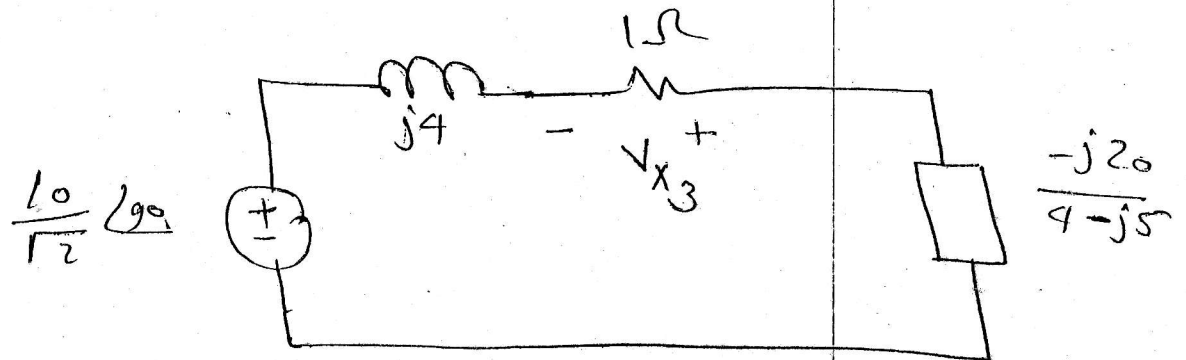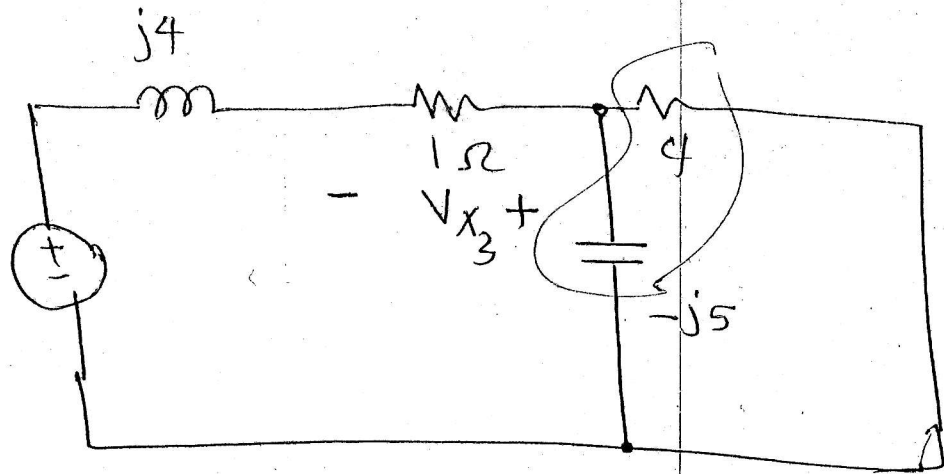

$$V_{X3} = -\frac{10}{\sqrt{2}} \angle 0^\circ \times \frac{1}{1+j4 - \frac{j20}{4-j5}}$$

⑧

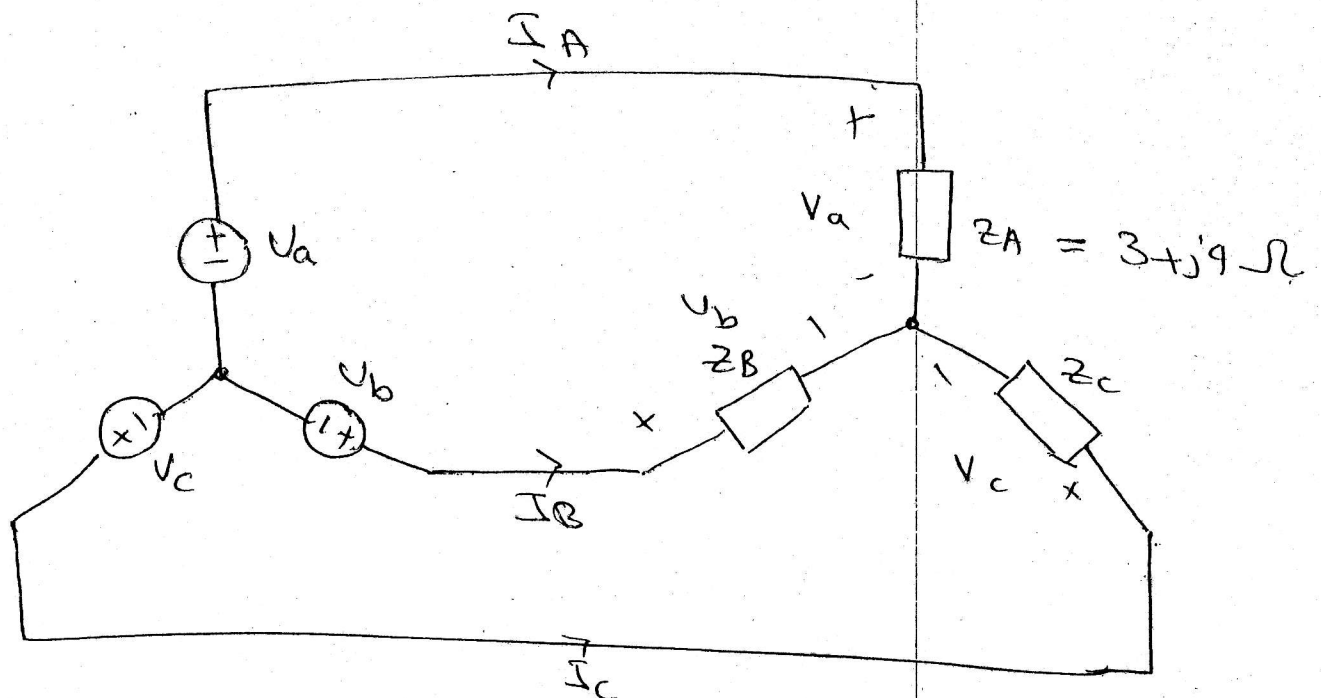

$$V_a = 240 \angle 0^\circ$$

$$V_b = 240 \angle -120^\circ$$

$$V_c = 240 \angle -240^\circ$$

$$I_A = I_a = \frac{240 \angle 0^\circ}{3 + j4} = \frac{240 \angle 0^\circ}{5 \angle 53.13^\circ} = 48 \angle -53.13^\circ$$

$$I_B = \frac{240 \angle -120^\circ}{5 \angle 53.13^\circ} = 48 \angle -173.13^\circ$$


$$I_C = I_c = \frac{240 \angle -240^\circ}{5 \angle 53.13^\circ} = 48 \angle -293.13^\circ$$

$$P.f. = \cos \theta_z$$

$$P.f. = 0.3$$

9

$$f_0 = 1 \text{ kHz}$$

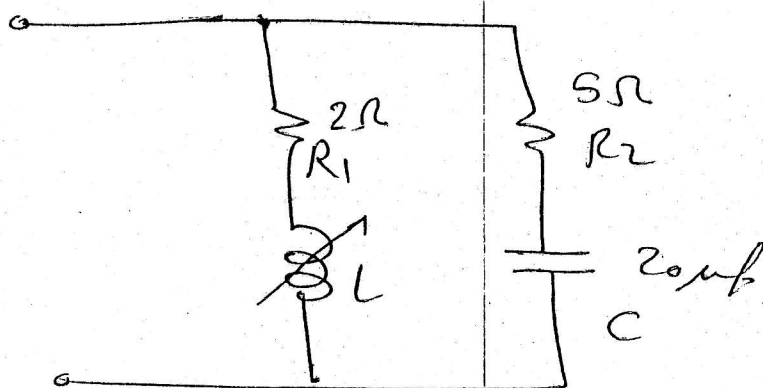

$$Y = \frac{1}{R_1 + j\omega L} + \frac{1}{R_2 + \frac{1}{j\omega C}}$$

$$Y = \frac{1}{R_1 + j\omega L} \left(\frac{R_1 - j\omega L}{R_1 - j\omega L} \right) + \frac{R_2 - \frac{1}{j\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}}$$

$$X = \frac{R_1 - j\omega L}{R_1^2 + \omega^2 L^2} + \frac{R_2 - \frac{1}{j\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}}$$

$$= \frac{R_1}{R_1^2 + \omega^2 L^2} - \frac{j\omega L}{R_1^2 + \omega^2 L^2} + \frac{R_2}{R_2^2 + \frac{1}{\omega^2 C^2}}$$

$$- \frac{\frac{1}{j\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}}$$

$$X = \left(\frac{R_1}{R_1^2 + \omega^2 L^2} + \frac{R_2}{R_2^2 + \frac{1}{\omega^2 C^2}} \right) - j \left(\frac{\omega L}{R_1^2 + \omega^2 L^2} + \frac{\frac{1}{\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}} \right)$$

$$\frac{\omega L}{R_1^2 + \omega^2 L^2} + \frac{\frac{1}{\omega C}}{R_2^2 + \frac{1}{\omega^2 C^2}} = 0$$

$$\therefore \omega_0 = 2\pi f_0 = 2\pi \times 1\text{kHz} = \underline{\hspace{2cm}}$$

$\underbrace{\hspace{10em}}_{L \text{ and } C}$